

# Basic Instrumentation Skills

## Lab Assignment #2

Ishmeet Singh

2020PHY1221

Unique Paper Code : 32223904

Course and Semester : B.Sc.(Hons.) Physics, Sem IV

Due Date : 6 Feb 2022

Submitted to : Dr. Daljeet Kaur

## Assignment 2: Q Meter Simulation

**Aim:** To determine accurate Quality Factor of an unknown coil.

**Apparatus:** VLAB IIT-KGP SIMULATOR

### Theory:

The determination of the storage factor  $Q$  is one of the most widely used means in the laboratory for testing radio frequency coils, inductors and capacitors.

The storage factor is equal to  $Q = \frac{w_o L}{R}$  where  $w_o$  is the resonant frequency,  $L$  is the inductance and  $R$  is the effective resistance of the a coil. The effective resistance  $R$ , is never determined directly since its value depends upon the value of frequency.

### PRINCIPAL OF WORKING:

The principle of working of this useful laboratory instrument is based upon the well-known characteristics of a resonant series  $R - L - C$  circuit.

At resonant frequency  $f_o$ , we have  $X_C = X_L$  where capacitive reactance  $X_C = \frac{1}{2\pi f_o C}$ , inductive reactance  $X_L = 2\pi f_o L$ , resonant frequency  $f_o = \frac{1}{2\pi\sqrt{LC}}$  and current at resonance  $I_o = \frac{E}{R}$ .

The voltage across the capacitor  $E_C = I_o \cdot X_C = I_o \cdot X_L = I_o \cdot w_o L$  and input voltage  $E = I_o \cdot R$  then  $\frac{E_C}{E} = \frac{w_o L}{R} = Q$  and  $E_C = QE$ .

If the input voltage is kept constant the voltage across capacitor is  $Q$  times  $E$  and a voltmeter connected across the capacitor can be calibrated to read the value of  $Q$  directly.

### Practical Circuit:

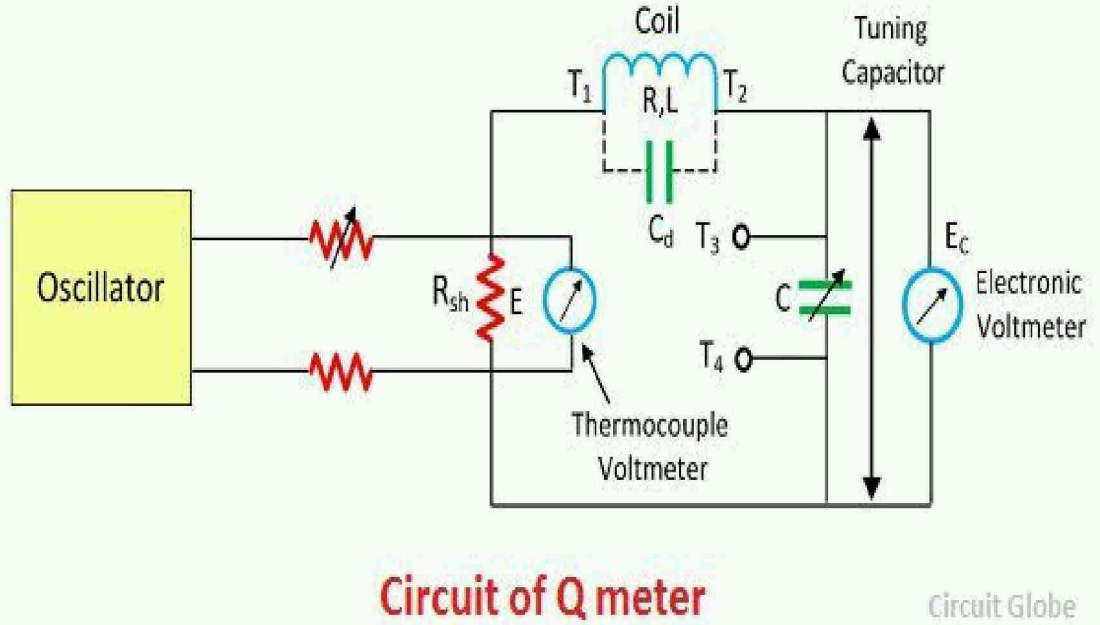


Figure 1: The Practical Circuit

The practical circuit is shown in Figure 1. It consists of self contained variable frequency RF oscillator. This oscillator delivers current to a low value shunt resistance  $R_{sh}$  : value may be  $0.02 \Omega$  The small value of input voltage  $E$  is injected into circuit that would be measured by thermocouple voltmeter. An electronic voltmeter is connected across this capacitor. The coil under test is connected to terminals  $T_1$  and  $T_2$ .

### Measurement of Q:

The circuit for measurement of  $Q$  shown in Figure 1. The oscillator is set to the desired frequency and then the tuning capacitor is adjusted for maximum value  $E_0$ . The input voltage  $E$  is kept constant then the voltage across capacitor is calibrated to read the value of  $Q$  directly. The measured value of  $Q$  is defined whole circuit not of the coil. There are errors caused due to shunt resistance and distributed capacitance of the circuit.

Correction of Shunt Resistance:

$$Q_{mes} = \frac{\omega_o L}{R + R_{sh}}$$
$$Q_{true} = \frac{\omega_o L}{R} = Q_{mes} \left(1 + \frac{R_{sh}}{R}\right)$$

Correction of Distributed Capacitance:

$$Q_{true} = Q_{mes} \left(1 + \frac{C_d}{C}\right)$$

Where,  $C_d$ =distributed capacitance and  $C$ = tuning capacitance.

Measurement of Self Capacitance:

The value of Inductance is given by  $L = \frac{1}{4\pi^2 f_o^2 C}$

The values of  $f_o$  and  $C$  are known and therefore the value of inductance may be calculated.

Measurement of Effective Resistance:

The value of effective resistance may be computed from the relation  $R = \frac{\omega_o L}{Q_{true}}$ .

Measurement of Self Capacitance:

The self capacitance is measured by making two measurements at different frequencies. The capacitor is set to a high value and the circuit is resonated by adjustment of the oscillator frequency. Resonance is indicated by the circuit Q meter. Let the values of tuning capacitor be  $C_1$  and that of frequency be  $f_1$  under these condition. Therefore,

$$f_1 = \frac{1}{2\pi \sqrt{L(C_1 + C_d)}}$$

The frequency is now increased to twice its initial value and the circuit is resonated again this time with the help of the tuning capacitor. Let the values of tuning capacitor be  $C_2$  and that of frequency be  $f_2$  under these condition. Therefore,

$$f_2 = \frac{1}{2\pi \sqrt{L(C_2 + C_d)}}$$

Now ,  $f_2 = 2.f_1$

The Distributed Capacitance,

$$C_d = \frac{C_1 - 4C_2}{3}$$

## Procedure:

- Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say 0.02 Ohm). Set all the parameters ( $R, L, C$ ) by yourself.
- Set the voltage value of the oscillator ( $E=10$  V).
- At  $f = 100\text{Hz}$ . Check the value of voltage drop across capacitor. ( $E_C$ ).
- Change the frequency until EC reach at the maximum value. Then calculate the value Q measured using this formula  $Q_{mes} = \frac{\omega_o L}{R+R_{sh}}$ .
- Calculate the true value of unknown coil by using this formula  $Q_{true} = \frac{\omega_o L}{R}$
- First resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C (say  $C_1$ ). Double the input frequency ( $f_1$ )(say  $f_2 = 2 * f_1$ ).Change the tuning capacitor value until resonance occurs. Note down the value of tuning capacitor C (say  $C_2$ ).Discharge capacitance( $C_d$ ) would be  $= \frac{C_1-4C_2}{3}$ .

## Observations:

### Values Given:

- $Voltage = 10V$
- $R_1 = 0\Omega$
- $R_{sh} = 0.02\Omega$
- $L = 5.277 \times 10^{-5}H$
- $R = 100\Omega$




For Frequency  $1 \times 10^6$  Hz:

## Q meter Experiment

### Procedure:

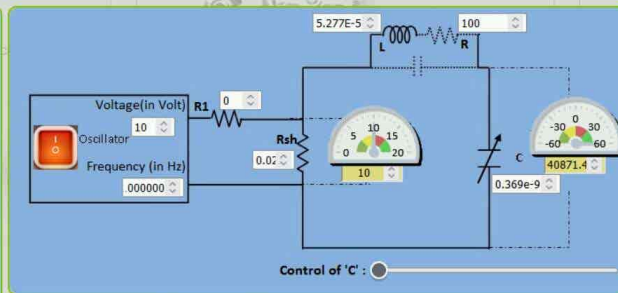1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$ pF ).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$ Mhz. Check the value of voltage drop across capacitor. (VC).
4. If  $V_c$  at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance ( $C_d$ ) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C. (say  $C_1$ ). Set the next resonance occurs at (say  $2*f_1$ ). Note down the value of tuning capacitor C. (say  $C_2$ ). Discharge capacitance ( $C_d$ ) would be  $= (C_1 - 4*C_2)/3$ .



Q measured    Q true    Discharge Capacitance

1. Switch on the above circuit.
2. Search for maximum 'Vc' at a particular 'f' by varying 'C'.
3. Then click on simulate to get the value of Q-measured.


Simulate

Vc (in volt): 40871.4    Vsh (in volt): 10    Q-Measured: 3.31434

## Q meter Experiment

### Procedure:

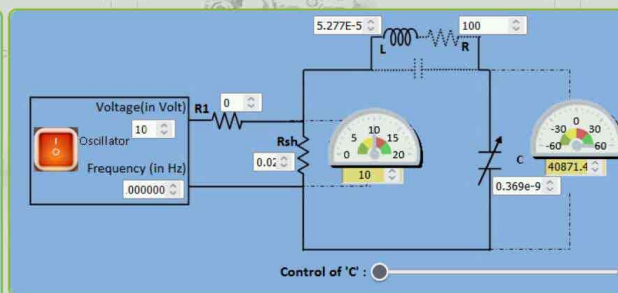1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$ pF ).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$ Mhz. Check the value of voltage drop across capacitor. (VC).
4. If  $V_c$  at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance ( $C_d$ ) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C. (say  $C_1$ ). Set the next resonance occurs at (say  $2*f_1$ ). Note down the value of tuning capacitor C. (say  $C_2$ ). Discharge capacitance ( $C_d$ ) would be  $= (C_1 - 4*C_2)/3$ .



Q measured    Q true    Discharge Capacitance

Click on the Simulate button to get the Q-True value.


Simulate

Q-True: 3.31501

## Q meter Experiment

### Procedure:

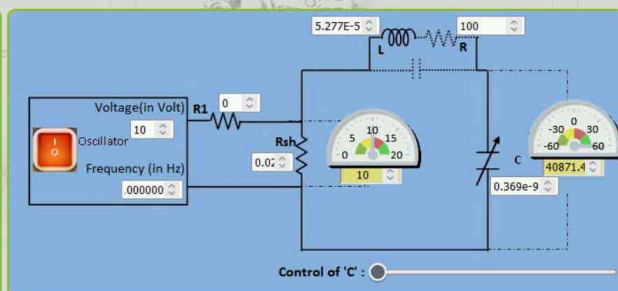1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$ pF ).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$ Mhz. Check the value of voltage drop across capacitor. (VC).
4. If  $V_c$  at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance ( $C_d$ ) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C. (say  $C_1$ ). Set the next resonance occurs at (say  $2*f_1$ ). Note down the value of tuning capacitor C. (say  $C_2$ ). Discharge capacitance ( $C_d$ ) would be  $= (C_1 - 4*C_2)/3$ .



Q measured    Q true    Discharge Capacitance

Click on the Simulate button to get the Discharge Capacitance value.

Simulate


Maximum Voltage at 'C', Vc (in volt): 40871.4  
Oscillator output, Vsh (in volt): 10  
Discharge Capacitance Cd: 2e-11

For Frequency  $1 \times 10^5$  Hz:

## Q meter Experiment

### Procedure:

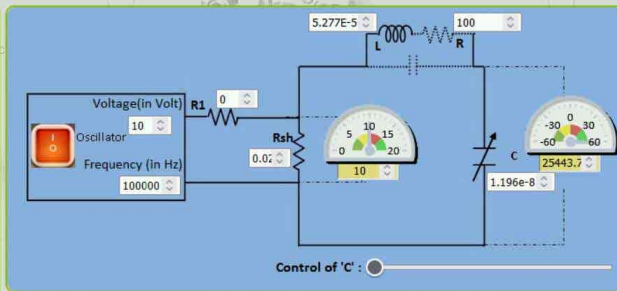1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$  pF).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$  Mhz. Check the value of voltage drop across capacitor. (VC).
4. If  $V_c$  at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance ( $C_d$ ) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C. (say  $C_1$ ). Set the next resonance occurs at (say  $2 \times f_1$ ). Note down the value of tuning capacitor C. (say  $C_2$ ). Discharge capacitance ( $C_d$ ) would be  $= (C_1 \cdot 4 \cdot C_2) / 3$ .



Q measured

Q true

Discharge Capacitance


1. Switch on the above circuit.
2. Search for maximum ' $V_c$ ' at a particular ' $f$ ' by varying ' $C$ '.
3. Then click on simulate to get the value of Q-measured.

Simulate

## Q meter Experiment

### Procedure:

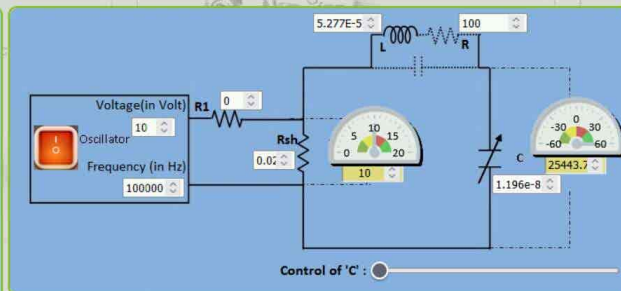1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$  pF).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$  Mhz. Check the value of voltage drop across capacitor. (VC).
4. If  $V_c$  at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance ( $C_d$ ) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C. (say  $C_1$ ). Set the next resonance occurs at (say  $2 \times f_1$ ). Note down the value of tuning capacitor C. (say  $C_2$ ). Discharge capacitance ( $C_d$ ) would be  $= (C_1 \cdot 4 \cdot C_2) / 3$ .



Q measured

Q true

Discharge Capacitance

Click on the Simulate button to get the Q-True value.


Q-True: 0.3315C

Simulate

## Q meter Experiment

### Procedure:

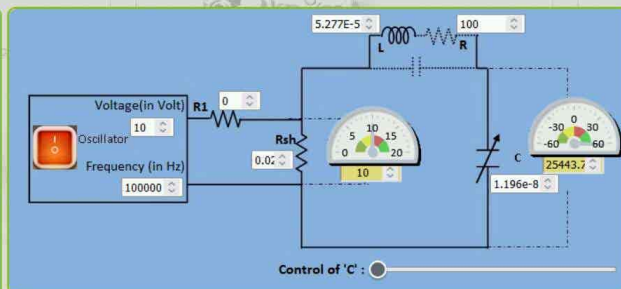1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$  pF).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$  Mhz. Check the value of voltage drop across capacitor. (VC).
4. If  $V_c$  at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance ( $C_d$ ) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say  $f_1$ ). Note down the value of tuning capacitor C. (say  $C_1$ ). Set the next resonance occurs at (say  $2 \times f_1$ ). Note down the value of tuning capacitor C. (say  $C_2$ ). Discharge capacitance ( $C_d$ ) would be  $= (C_1 \cdot 4 \cdot C_2) / 3$ .



Q measured

Q true

Discharge Capacitance

Click on the Simulate button to get the Discharge Capacitance value.

Maximum Voltage at ' $C$ ',  $V_c$  (in volt): 25443.7

Oscillator output,  $V_{sh}$  (in volt): 10

Discharge Capacitance  $C_d$ : 2e-11

Simulate




For Frequency  $9 \times 10^5$  Hz:

## Q meter Experiment

### Procedure:

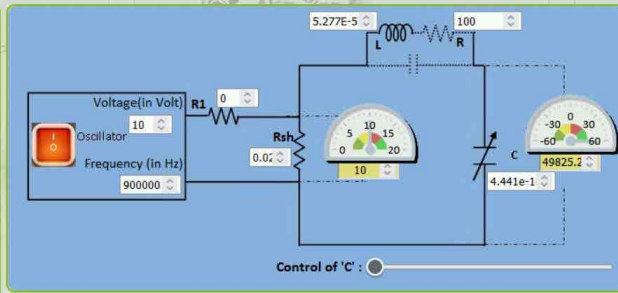1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$  pF ).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$  Mhz. Check the value of voltage drop across capacitor. (VC).
4. If Vc at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance (Cd) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say f1). Note down the value of tuning capacitor C. (say C1). Set the next resonance occurs at (say  $2 \times f_1$ ). Note down the value of tuning capacitor C. (say C2). Discharge capacitance (Cd) would be  $=(C1 \cdot 4 \cdot C2)/3$ .



Q measured

Q true

Discharge Capacitance

1. Switch on the above circuit.
2. Search for maximum 'Vc' at a particular 'f' by varying 'C'.
3. Then click on simulate to get the value of Q-measured.


Simulate

Vc (in volt): 4.441E-1 Vsh (in volt): 10 Q-Measured: 2.98291

## Q meter Experiment

### Procedure:

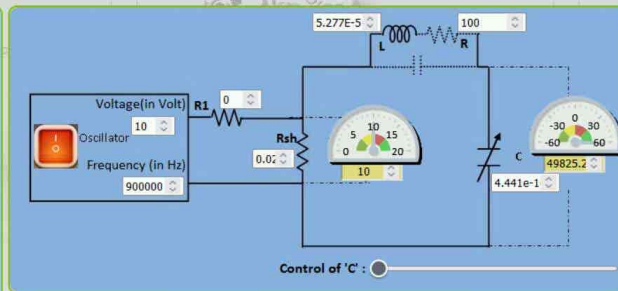1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$  pF ).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$  Mhz. Check the value of voltage drop across capacitor. (VC).
4. If Vc at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance (Cd) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say f1). Note down the value of tuning capacitor C. (say C1). Set the next resonance occurs at (say  $2 \times f_1$ ). Note down the value of tuning capacitor C. (say C2). Discharge capacitance (Cd) would be  $=(C1 \cdot 4 \cdot C2)/3$ .



Q measured

Q true

Discharge Capacitance

Click on the Simulate button to get the Q-True value.


Simulate

Q-True: 2.98351

## Q meter Experiment

### Procedure:

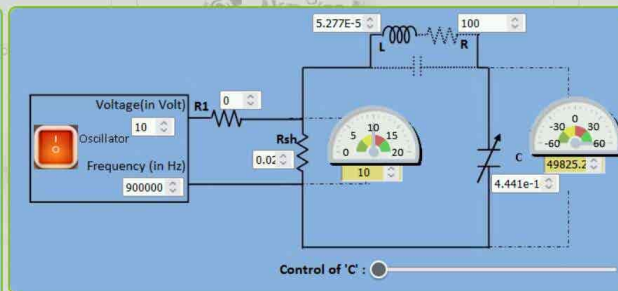1. Set the Shunt Resistance ( $R_{sh}$ ) value as small as possible (Say=0.02 Ohm). Set all the parameters of unknown coil. A sample parameters may be this (Say,  $L=5.277 \times 10^{-5}$ ,  $R=100$ ,  $C_d=20$  pF ).
2. Set the voltage value of the oscillator ( $V=10$  V).
3. At  $f=1$  Mhz. Check the value of voltage drop across capacitor. (VC).
4. If Vc at maximum during resonance, click simulate to measured the value of Q meter. Else change the frequency.
5. Find Q true value by changing the tab to "Q true".
6. Find Discharge capacitance (Cd) from "Discharge capacitance" tab: 1st resonance occurs due to frequency (say f1). Note down the value of tuning capacitor C. (say C1). Set the next resonance occurs at (say  $2 \times f_1$ ). Note down the value of tuning capacitor C. (say C2). Discharge capacitance (Cd) would be  $=(C1 \cdot 4 \cdot C2)/3$ .



Q measured

Q true

Discharge Capacitance

Click on the Simulate button to get the Discharge Capacitance value.

Simulate

Maximum Voltage at 'C', Vc (in volt): 4.441E-1

Oscillator output, Vsh (in volt): 10

Discharge Capacitance Cd: 2E-11



## Calculations:

1. For Frequency  $1 \times 10^6 Hz$  :

$$Q_{mes} = 3.31434$$

$$Q_{true} = 3.31501$$

$$\text{Absolute Error in } Q_{mes} = Q_{true} - Q_{mes}$$

$$= 3.31501 - 3.31434$$

$$= 0.00067$$

$$\text{Relative Error in } Q_{mes} = \frac{Q_{true} - Q_{mes}}{Q_{true}}$$

$$= \frac{3.31501 - 3.31434}{3.31501}$$

$$= 0.000202111$$

$$\text{Relative percentage Error in } Q_{mes} = \frac{Q_{true} - Q_{mes}}{Q_{true}} \times 100$$

$$= \frac{3.31501 - 3.31434}{3.31501} \times 100$$

$$= 0.02\%$$

2. For Frequency  $1 \times 10^5 Hz$  :

$$Q_{mes} = 0.33143$$

$$Q_{true} = 0.33150$$

$$\text{Absolute Error in } Q_{mes} = Q_{true} - Q_{mes}$$

$$= 0.33150 - 0.33143$$

$$= 0.00007$$

$$\text{Relative Error in } Q_{mes} = \frac{Q_{true} - Q_{mes}}{Q_{true}}$$

$$= \frac{0.33150 - 0.33143}{0.33150}$$

$$= 0.000211161$$

$$\begin{aligned}
\text{Relative percentage Error in } Q_{mes} &= \frac{Q_{true} - Q_{mes}}{Q_{true}} \times 100 \\
&= \frac{0.33150 - 0.33143}{0.33150} \times 100 \\
&= 0.02\%
\end{aligned}$$

3. For Frequency  $9 \times 10^5 Hz$  :

$$Q_{mes} = 2.98291$$

$$Q_{true} = 2.98351$$

$$\text{Absolute Error in } Q_{mes} = Q_{true} - Q_{mes}$$

$$= 2.98351 - 2.98291$$

$$= 0.0006$$

$$\text{Relative Error in } Q_{mes} = \frac{Q_{true} - Q_{mes}}{Q_{true}}$$

$$= \frac{2.98351 - 2.98291}{2.98351}$$

$$= 0.0002011054$$

$$\text{Relative percentage Error in } Q_{mes} = \frac{Q_{true} - Q_{mes}}{Q_{true}} \times 100$$

$$= \frac{2.98351 - 2.98291}{2.98351} \times 100$$

$$= 0.02\%$$

## Results:

1. For Frequency  $1 \times 10^6 Hz$  :

- $V_C = 40871.4V$
- $V_{sh} = 10V$
- $Q_{mes} = 3.31434$
- $Q_{true} = 3.31501$
- $C_d = 2 \times 10^{-11}$
- Absolute Error in  $Q_{mes} = 0.00067$
- Relative Error in  $Q_{mes} = 0.000202111$
- Relative Percentage error in  $Q_{mes} = 0.02\%$

2. For Frequency  $1 \times 10^5 Hz$  :

- $V_C = 25443.7V$
- $V_{sh} = 10V$
- $Q_{mes} = 0.33143$
- $Q_{true} = 0.33150$
- $C_d = 2 \times 10^{-11}$
- Absolute Error in  $Q_{mes} = 0.00007$
- Relative Error in  $Q_{mes} = 0.000211161$
- Relative Percentage error in  $Q_{mes} = 0.02\%$

3. For Frequency  $9 \times 10^5 \text{ Hz}$  :

- $V_C = 49825.2V$
- $V_{sh} = 10V$
- $Q_{mes} = 2.98291$
- $Q_{true} = 2.98351$
- $C_d = 2 \times 10^{-11}$
- Absolute Error in  $Q_{mes} = 0.0006$
- Relative Error in  $Q_{mes} = 0.0002011054$
- Relative Percentage error in  $Q_{mes} = 0.02\%$